




**PAMANTASAN NG LUNGSOD NG MAYNILA**  
(University of the City of Manila)  
Intramuros, Manila

---

 **Microprocessor Lab**

Laboratory Activity No. 1  
**Familiarization with TinkerCAD**



Score

*Submitted by:*  
**Gomez, Ericka Mae S.**  
**<Saturday 1:00-7:00pm> / <CpE 412-2>**

*Date Submitted*  
**09-16-2023**

*Submitted to:*  
**Engr. Maria Rizette H. Sayo**


---

## 1. Exercise

- A process in Tinkercad where we can develop electronic circuits that can be quickly updated, modified and tested is called **Prototyping Process**
- In Tinkercad, **The Start/Stop Simulation** tests the working of the circuits and the components.
- The device used to assemble and connect the various components is known as **breadboard**
- In an electronic circuit with LED, the positive end of the circuit should be connected to **anode** and negative end should be connected to **cathode** of the LED.
- A **resistor** is used to restrict the flow of current to electrical components
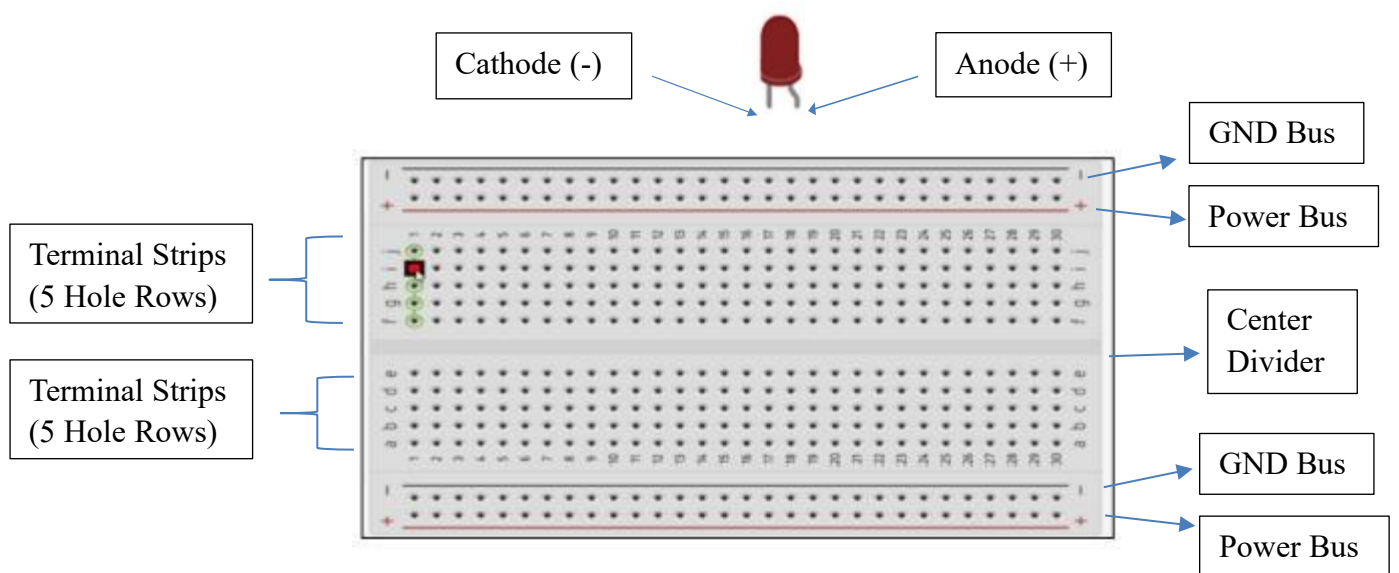
## 2. Label the following:

- Anode and Cathode in a LED
- Different parts of breadboard



- List the electronic components used in a circuit assembly
  - Breadboard
  - Arduino uno R3
  - LED
  - Resistor (1k ohms)
  - Jumper wires
  - Potentiometer (Analog I/O)